

REPORT

COURSE: CSE - 206

EXPERIMENT NO: 4

TOPIC: Comparator, Adder/ Subtractor

SUBMITTED BY:

1805021 - Abdus Samee

1805022 - Md. Tamimul Ehsan

1805023 - Mohammad Abrarul Hasanat

1805024 - Zannatul Naim

1805025 - Md. Fahim Shahriar

Problem - 1

Problem Specification:

Design using basic gates, a 2-bit comparator to compare 2-bit numbers X and Y. The circuit should provide 3 output lines to indicate $X > Y$, $X = Y$, and $X < Y$.

Required Instruments:

(1) 4 input pins, (2) 3 output pins, (3) 1 IC7404 gate, (4) 4 IC7408 gates, (5) 2 IC7432 gates, (6) Wires.

Truth Table:

X		Y		Output		
P	Q	R	S	$A(X < Y)$	$B(X = Y)$	$C(X > Y)$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0

1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

Minimized equation:

For $A(X < Y)$, we construct the K-map below:

		RS			
		00	01	11	10
PQ	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	1	0

The simplified equation we get from the K-map is: $P'R + Q'RS + P'Q'S$

For $B(X=Y)$, we construct the K-map below:

		RS			
		00	01	11	10
PQ	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

The simplified equation we get from K-map is:

$$\begin{aligned}
 &P'Q'R'S' + P'QR'S + PQRS + PQ'RS' \\
 &= P'R'(Q'S' + QS) + PR(Q'S' + QS) \\
 &= (PR + P'R')(QS + Q'S') \\
 &= (P \odot R)(Q \odot S)
 \end{aligned}$$


For $C(X>Y)$, we construct the K-map below:

		RS			
		00	01	11	10
PQ	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

The simplified equation we get from K-map is:

$$PR' + QR'S' + PQS'$$

Circuit Diagram:

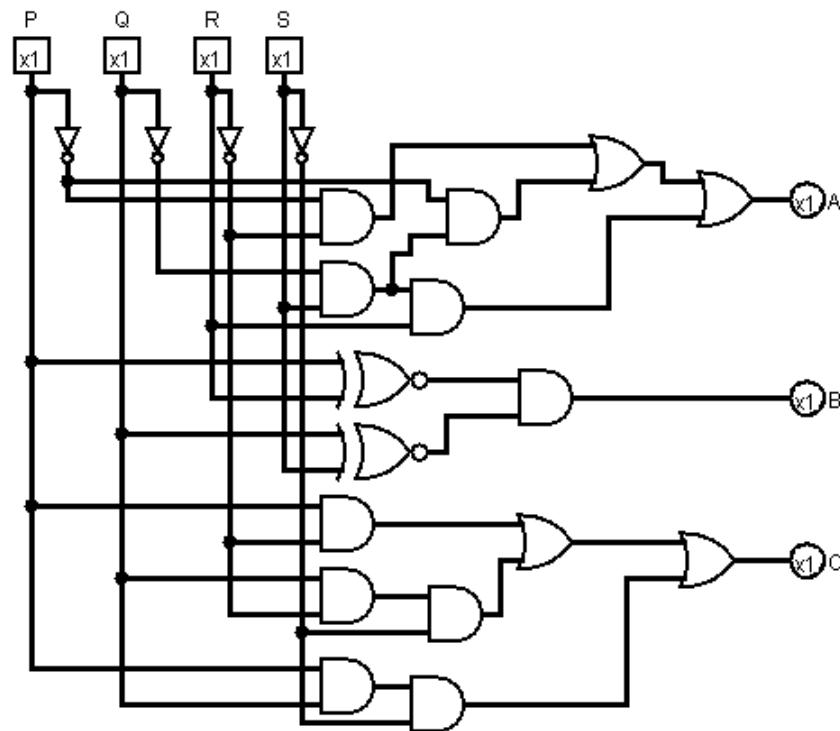

Problem - 2

Problem Specification:

Design a 1-bit full subtractor circuit using basic logic gates. Inputs are P, Q, and R denoting minuend, subtrahend, and previous borrow respectively. The outputs are D and B representing the difference and output borrow.

Required Instruments:

(1) 3 input pins, (2) 2 output pins, (3) IC7404 gate, (4) IC7408 gate, (5) IC7432 gate, (6) Wires.

Truth Table:

P	Q	R	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Minimized equation:

For D, we draw the K-map below:

		QR			
		00	01	11	10
P	0	0	1	0	1
	1	1	0	1	0

The simplified equation we get from the above K-map is:

$$\begin{aligned}D &= P'Q'R + P'QR' + PQ'R' + PQR \\ \text{or, } D &= P'(Q'R + QR') + P(QR + Q'R') \\ \text{or, } D &= P'(Q \oplus R) + P(Q \odot R) \\ \text{or, } D &= P \oplus Q \oplus R\end{aligned}$$

For B, we draw the K-map below:

		QR			
		00	01	11	10
P	0	0	1	1	1
	1	0	0	1	0

The simplified equation we get from the above K-map is:

$$B = P'R + QR + P'Q$$

Circuit Diagram:

